

Automatic stair lights

Photocells S1 and S2 drive the instructions RS1, RS2, R1, R2, TC1, TC2, CTU, CTD. Depending on your walking direction, the instructions RS1, R1, TC1, CTU, otherwise RS2, R2, TC2, CTD will work.

Photocells S3 and S4 drive the instructions RS3, RS4, R3, R4, TC3, TC4, CTU, CTD. The count is performed by the "relays" from 1 to 5. It increases by the instruction CTU and decreases by the instruction CTD.

Lights from L1 to L10 are controlled by timers from T1 to T10. Lights from L10 to L1 are controlled by timers from T1A to T10A.













